

L5 - RC FILTERS

PHYS 301: ANALOG AND DIGITAL ELECTRONICS

MATTHEW FERGUSON


ISAAC WOODARD

DECEMBER 2, 2020

REVIEW

IMPEDANCE

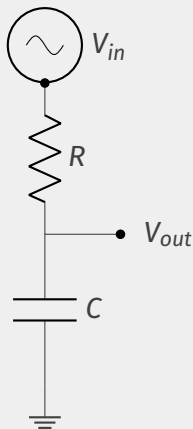

$$Z_R = R$$


$$Z_C = \frac{1}{j\omega C}$$


$$Z_L = j\omega L$$

$$\omega = 2\pi f$$

RC VOLTAGE DIVIDER (AC)




$$V_{out} = \frac{Z_C}{R + Z_C} V_{in}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$



$$\Delta\phi = -\tan^{-1}(\omega RC)$$

FILTERS

MIXED FREQUENCIES

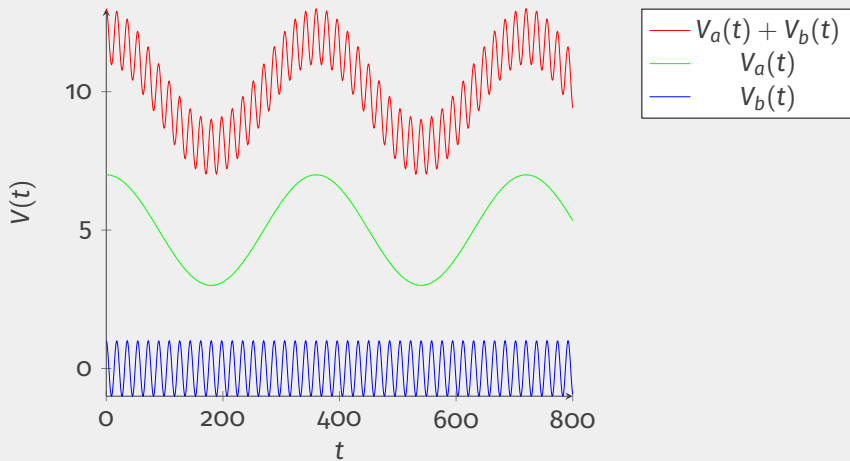

LOW PASS FILTER

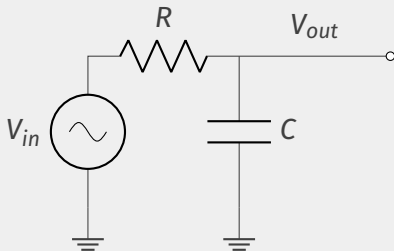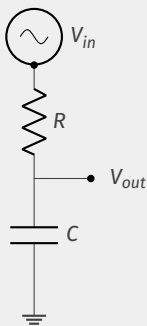

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\Delta\phi = -\tan^{-1}(\omega RC)$$

DECIBEL SCALE


- Used as a logarithmic power scale
- Can be applied to voltage gain

$$dB = 10 \log \left| \frac{V_{out}}{V_{in}} \right|^2$$

or

$$dB = 20 \log \left| \frac{V_{out}}{V_{in}} \right|$$

BODE MAGNITUDE PLOT

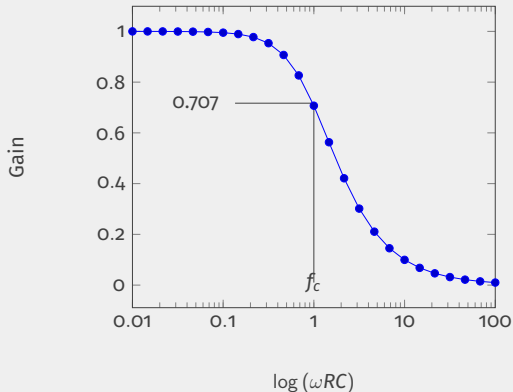

$$f_c = f_{-3dB} = \frac{1}{2\pi RC}$$

$$\begin{aligned} \text{Gain} &= \frac{1}{\sqrt{2}} \\ &= \frac{1}{\sqrt{1 + (\omega RC)^2}} \\ &= \frac{1}{\sqrt{1 + 1}} \end{aligned}$$

CRITICAL POINT

$$f_c, \quad f_{-3dB}$$

$$\omega_c RC = 1 \rightarrow \omega_c = \frac{1}{RC} \rightarrow f_c = \frac{1}{2\pi RC}$$


$$dB = 20 \log \left| \frac{V_{out}}{V_{in}} \right|$$

$$dB_{\frac{1}{2}} = 20 \log \left| \frac{1}{\sqrt{2}} \right| = -10 \log 2 = -3.03 \text{ dB}$$


BODE TABLE

f	V_{in}	V_{out}	$Gain$	$\Delta\phi$
1Hz				
\vdots				
100kHz				

BODE PHASE PLOT

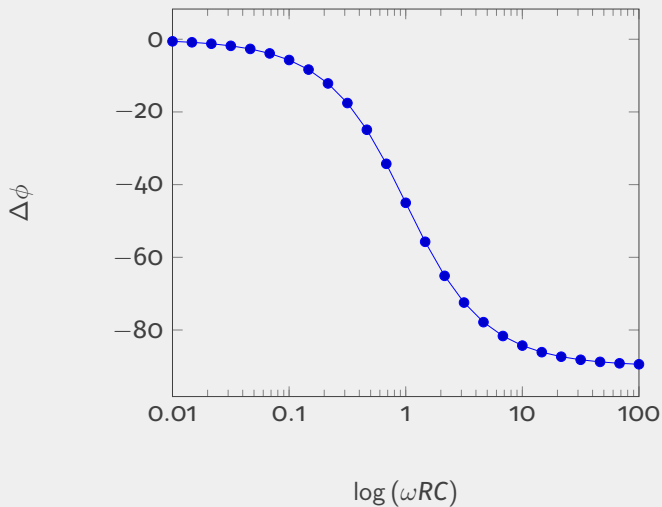



HIGH PASS FILTER

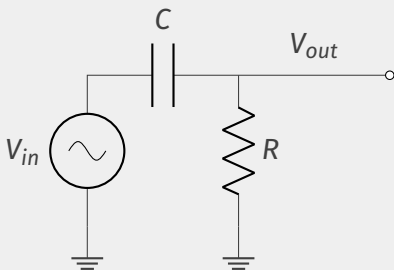


$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

$$\Delta\phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

HIGH PASS BODE PLOTS

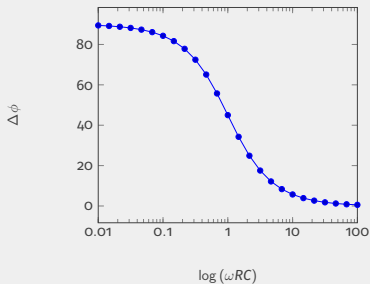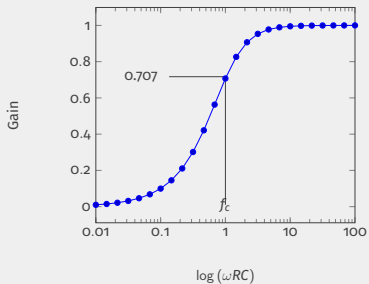

BLOCKING CAPACITOR

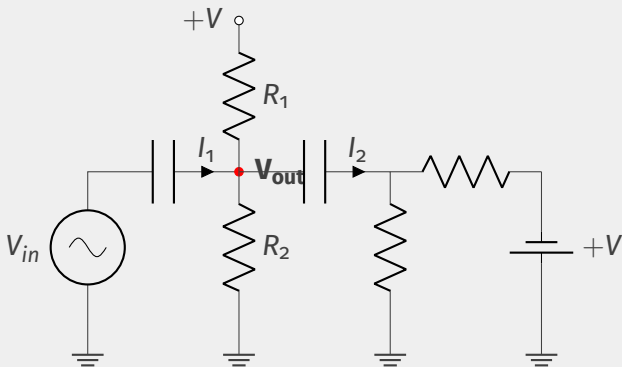

$$V_{out} = \frac{R_2}{R_1 + R_2} V + V_{in} - \frac{I_1}{j\omega C}$$